

National Exams December 2010  
04-BS-4 Electric Circuits and Power

3 hours duration

Notes:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of assumptions made;
2. Candidates may use one of two calculators, a Casio or Sharp approved models. This is a Closed Book exam. One aid sheet written on both sides is permitted.
3. Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.
4. All questions are of equal value.

Marking Scheme

- Question 1: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 2: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 3: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 4: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 5: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 6: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 7: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.

**Question 1**

In the DC circuit of Figure 1 assume the following:  $R_1 = 5\ \Omega$ ,  $R_2 = 6\ \Omega$ ,  $R_3 = 3\ \Omega$ ,  $R_4 = 3\ \Omega$ ,  $R_5 = 6\ \Omega$ ,  $I_s = 2\ \text{A}$ , and  $V_s = 3\ \text{V}$ .

- Write Kirchhoff's Current Law (KCL) equations for nodes A, B, C, and D;
- Write Kirchhoff's Voltage Law (KVL) equations for loops ABCA and BCDB;
- Calculate current through the resistor  $R_1$ ;
- Calculate power generated by the current source  $I_s$ .

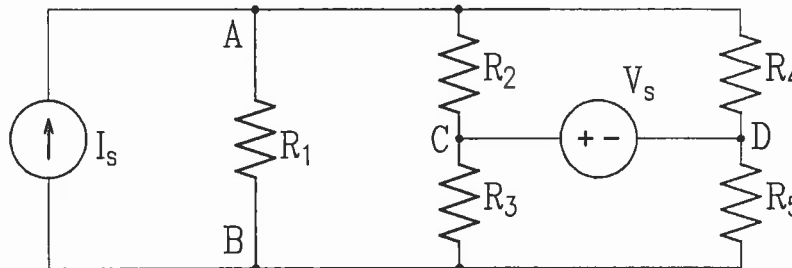


Figure 1: Circuit diagram for Question 1

**Question 2**

Consider the circuit of Figure 2. Known parameters are:  $R_1 = 50\ \Omega$ ,  $R_2 = 100\ \Omega$ ,  $R_3 = 50\ \Omega$ ,  $R_4 = 100\ \Omega$ ,  $R_5 = 100\ \Omega$ ,  $R_6 = 40\ \Omega$ ,  $R_7 = 60\ \Omega$ ,  $V_{s1} = 30\ \text{V}$  and  $V_{s2} = 5\ \text{V}$ . Determine the following:

- Thevenin equivalent voltage seen by the load;
- Thevenin equivalent resistance seen by the load;
- What is the load resistance corresponding to the maximum power transfer to  $R_L$ ?  
What is the maximum power transferred to  $R_L$ ?
- What is the power transferred to the load, if the load resistance is  $R_L = 64\ \Omega$ .

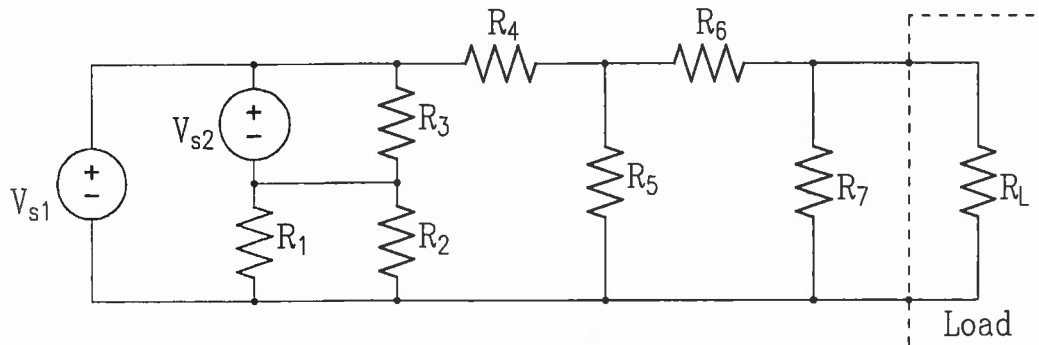


Figure 2: Circuit diagram for Question 2

**Question 3**

In the circuit of Figure 3  $R_1 = 3 \text{ k}\Omega$ ,  $R_2 = 3 \text{ k}\Omega$ ,  $R_3 = 6 \text{ k}\Omega$ ,  $R_4 = 18 \text{ k}\Omega$ ,  $C_1 = 10 \mu\text{F}$ ,  $C_2 = 3 \mu\text{F}$ ,  $C_3 = 6 \mu\text{F}$ , and  $I_s = 200 \text{ mA}$ . The switch is in position 0. At  $t = 0 \text{ s}$ , the switch moves to position 1. At  $t = 5 \text{ s}$ , the switch moves to position 2. Assume that none of the capacitors has any stored energy at  $t = 0 \text{ s}$ .

- Calculate the time constant of the circuit when the switch is in position 1;
- Calculate the voltage across the capacitor  $C_1$  at  $t = 1 \text{ s}$ .
- Plot waveform of the current  $i_1(t)$  from  $t = -10 \text{ ms}$  to  $t = 200 \text{ ms}$ ;
- What is the total energy stored in all three capacitors at  $t = 6 \text{ s}$ .

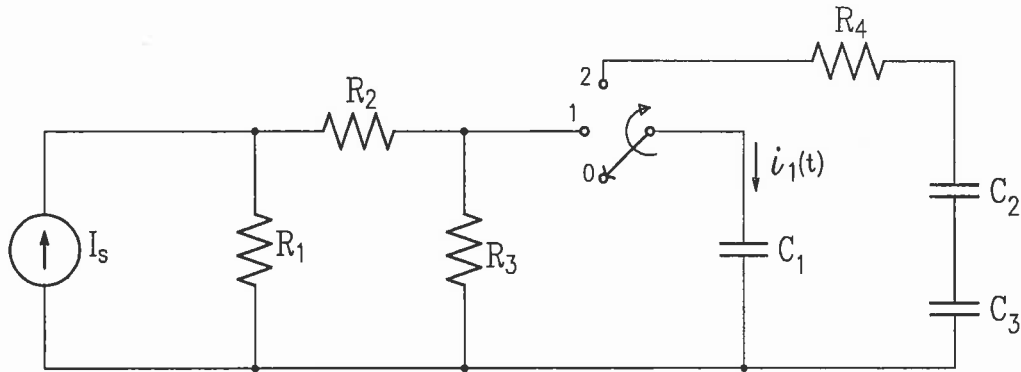


Figure 3: Circuit diagram for Question 3

**Question 4**

In the circuit of Figure 4 assume the following:  $L_1 = 160 \text{ mH}$ ,  $L_2 = 80 \text{ mH}$ ,  $R = 2 \Omega$ ,  $C = 20 \text{ mF}$ ,  $v_{s1}(t) = \sqrt{2} 10 \cos(25t + \frac{\pi}{4}) \text{ V}$ , and  $v_{s2}(t) = 10 \cos(25t) \text{ V}$ . Assume that the circuit is in a steady-state operating condition. Calculate the following:

- Impedances  $Z_{L1}$ ,  $Z_{L2}$ , and  $Z_C$ ;
- Voltage phasor  $V_1$ ;
- Current phasors  $I_{L1}$  and  $I_{L2}$ ;
- Resistor current in time-domain,  $i_R(t)$ .

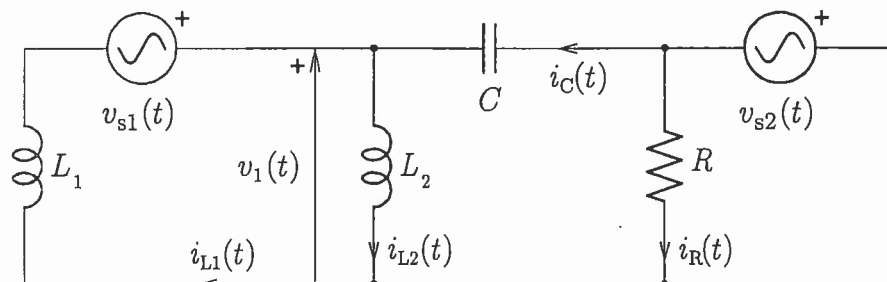


Figure 4: Circuit diagram for Question 4

**Question 5**

In the circuit of Figure 5, parameters are:  $R = 10\ \Omega$ ,  $L_1 = 10\ \text{mH}$ ,  $L_2 = 5\ \text{H}$ ,  $C_1 = 10\ \mu\text{F}$ ,  $C_2 = 200\ \text{pF}$ , and  $v_s(t) = 100 \cos(\omega t)\ \text{V}$ .

- Assume that the source frequency is 60 Hz. Calculate active and reactive power supplied by the source when S is in position 1.
- Determine the source frequency so that the source current amplitude is maximal when S is in position 1. What is this frequency called?
- For the frequency calculated under (b) determine the reactive power supplied by the source and the expression for current  $i_1(t)$ .
- When S is in position 2: Determine the source frequency so that the reactive power supplied by the source is zero. Determine expressions for currents  $i_2(t)$  and  $i_{2L}(t)$ .

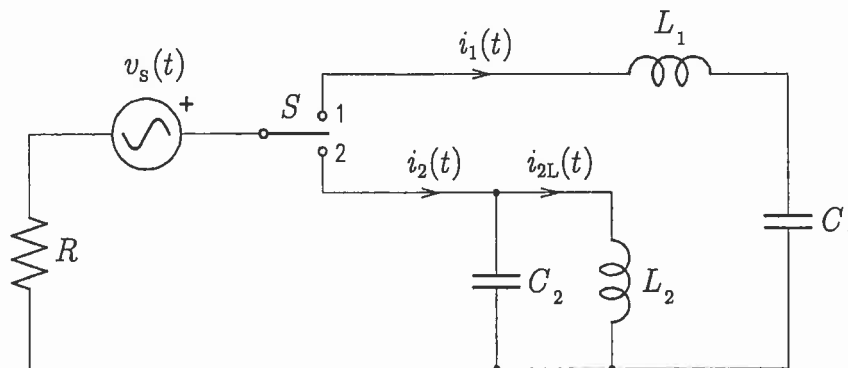


Figure 5: Circuit diagram for Question 5

**Question 6**

A half-wave diode rectifier is used to provide a DC current to a  $50\ \text{k}\Omega$  resistive load. Rectifier is supplied by an ideal AC voltage source (50 Hz,  $20\ \text{V}_{\text{RMS}}$ ).

- Draw the rectifier schematic diagram. Sketch the input voltage, the output voltage, the output current, and the current through each of the rectifier diodes.
- Find the peak and the average current in the load.
- Sketch the input and the output voltage, if the rectifier diode has on-state voltage drop of 0.4 V.
- Using a  $50\ \Omega$  resistance, design an RC low-pass filter (for DC side) that can attenuate a 100 Hz sinusoidal voltage by 20 dB with respect to the DC gain.

**Question 7**

A logic platform provides the wind turbine blade pitch (angle) control. To operate, it uses the following sensors:

- A) *Emergency stop* switch (1 if pressed)
- B) Limit switch for *Full-speed* position (1 if reached)
- C) Limit switch for *Vane* position (1 if reached)
- D) Turbine *Ready* signal(1 if ready)
- E) Wind speed upper limit (1 if wind speed is too high)
- F) Wind speed lower limit (1 if wind speed is too low)
- G) Rotor speed limit (1 if rotor speed is too high)

The wind turbine rotor blades should be in *Vane* position when the turbine is not operational and should be in *Full-speed* position under normal operating conditions. Rotor blade pitch is achieved by means of special servo motors that respond to commands:

- a) Up (initiate blade movement toward *Full-speed* position)
- b) Down (initiate normal blade movement toward *Vane* position)
- c) Fast Down (initiate fast blade movement toward *Vane* position)

The *Emergency Stop Condition* is when the wind speed is too high, turbine is not *Ready*, or *Emergency stop* button is pressed. When emergency stop condition is detected blades should move fast to *Vane* position.

Rotor speed should never exceed the maximum rotor speed. If the maximum rotor speed limit is reached, the blade should move toward *Vane* position. The blade movement should stop when the rotor speed drops below the speed limit.

If the wind speed is too low, and turbine is ready, blades should move to *Vane* position.

Neglect the changing wind conditions.

- a) Design a logic circuit that initiates normal start and brings blades to *Full-speed* position.
- b) Design a logic circuit that handles the *Emergency Stop Condition*.
- c) Design a logic circuit that assures that the turbine speed does not exceed the speed limit.
- d) Design a logic circuit that initiates normal stop due to too low wind speed.

**Note:**

All kinds of gates could be used to construct the logic circuits.