

National Exams May 2011  
04-BS-4 Electric Circuits and Power

3 hours duration

Notes:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of assumptions made;
2. Candidates may use one of two calculators, a Casio or Sharp approved models. This is a Closed Book exam. One aid sheet written on both sides is permitted.
3. Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.
4. All questions are of equal value.

Marking Scheme

- Question 1: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 2: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 3: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 4: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 5: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 6: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 7: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.

**Question 1**

In the DC circuit of Figure 1 assume the following:  $R_1 = 3 \Omega$ ,  $R_2 = 6 \Omega$ ,  $R_3 = 15 \Omega$ ,  $R_4 = 8 \Omega$ ,  $R_5 = 6 \Omega$ , and  $V_s = 24 \text{ V}$ . It is observed that  $I_5 = 2 \text{ A}$ .

- Write Kirchhoff's Current Law (KCL) equations for nodes A, B, and C;
- Write Kirchhoff's Voltage Law (KVL) equations for loops  $R_1R_3R_o$  and  $R_1V_sR_5R_o$ ;
- Calculate voltage  $V_{BD}$  and current  $I_3$  ;
- Calculate  $R_o$ ,  $I_o$  and the power dissipated in resistor  $R_o$ .

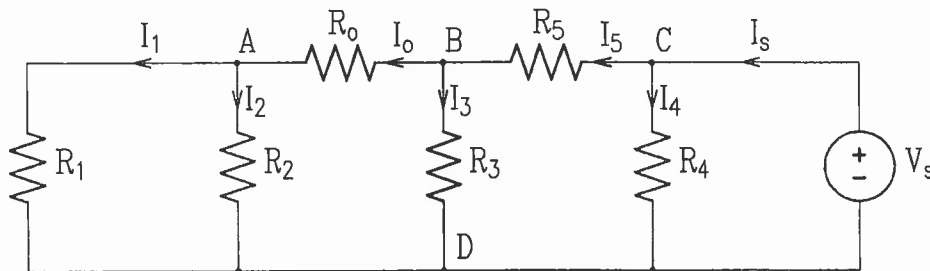


Figure 1: Circuit diagram for Question 1

**Question 2**

Consider the circuit of Figure 2. Known parameters are:  $R_1 = 12.5 \text{ M}\Omega$ ,  $R_2 = 22.5 \text{ k}\Omega$ ,  $R_3 = 300 \text{ k}\Omega$ ,  $R_4 = 100 \text{ k}\Omega$ ,  $R_5 = 10 \text{ k}\Omega$ ,  $R_6 = 10 \text{ k}\Omega$ ,  $R_7 = 5 \text{ k}\Omega$ , and  $V_s = 20 \text{ V}$ . Determine the following:

- Thevenin equivalent resistance seen by the load;
- Thevenin equivalent voltage seen by the load;
- Power transferred to the load if the load resistance is  $R_L = 100 \Omega$ .
- Determine the load resistance for the maximum power transfer. Determine the power transferred to the load in this case.

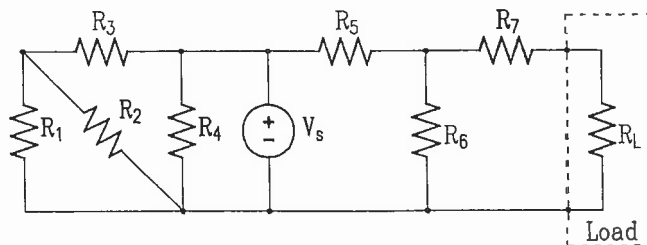


Figure 2: Circuit diagram for Question 2

**Question 3**

In the circuit of Figure 3  $R_1 = 3\ \Omega$ ,  $R_2 = 3\ \Omega$ ,  $R_3 = 6\ \Omega$ ,  $R_4 = 4\ \Omega$ ,  $R_5 = 4\ \Omega$ ,  $R_6 = 8\ \Omega$ ,  $L = 20\ \text{mH}$ , and  $V_s = 12\ \text{V}$ . The switch  $S$  is closed for a long time. At  $t = 0\ \text{s}$ , the switch  $S$  opens.

- Calculate the voltage across the resistor  $R_4$  and the inductor current in steady-state while the switch  $S$  is closed.
- What is the energy stored in the inductor at  $t = 0_-\ \text{s}$ .
- Calculate the time constant of the circuit when the switch is open;
- Plot the current  $I_L(t)$  from  $t = -5\ \text{ms}$  to  $t = 25\ \text{ms}$ ;

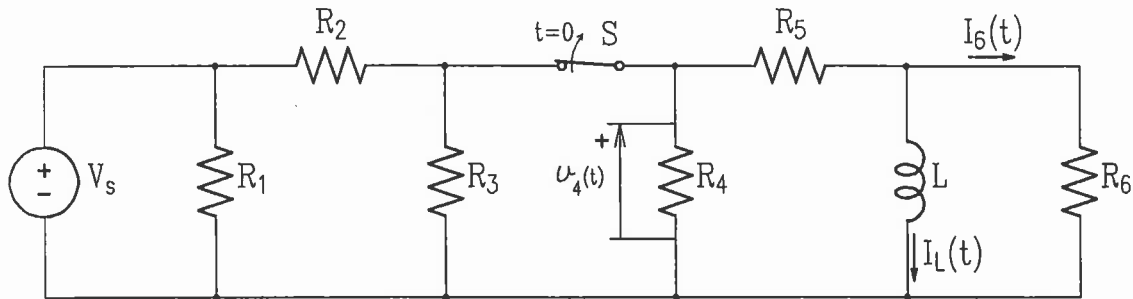


Figure 3: Circuit diagram for Question 3

**Question 4**

In the circuit of Figure 4 assume the following:  $L_1 = 160\ \text{mH}$ ,  $L_2 = 80\ \text{mH}$ ,  $R_1 = 5\ \Omega$ ,  $R_2 = 2\ \Omega$ ,  $C = 20\ \text{mF}$ , and  $v_s(t) = \sqrt{2} 10 \cos(100t)\ \text{V}$ . Assume that the circuit is in a steady-state operating condition. Calculate the following:

- Impedances  $Z_{L1}$ ,  $Z_{L2}$ , and  $Z_C$ ;
- Voltage phasor  $V_1$ ;
- Current phasor  $I_1$ ;
- Capacitor current in time-domain.

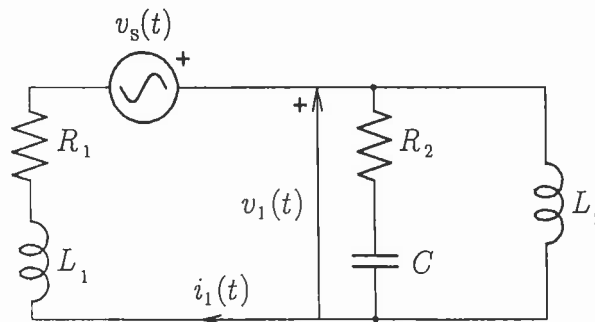


Figure 4: Circuit diagram for Question 4

**Question 5**

In the circuit of Figure 5, parameters are:  $R_1 = 120 \Omega$ ,  $R_2 = 13 \Omega$ ,  $L_1 = 19 \text{ mH}$ ,  $L_2 = 3 \text{ H}$ ,  $C = 220 \text{ pF}$ ,  $V_{s1}(t) = 24 \cos(\omega t) \text{ V}$ .

- Determine the source frequency so that current  $I_1(t)$  and voltage  $V_2(t)$  are in phase.
- What is the frequency of (a) called? Does any other frequency have the same property in the circuit of Figure 5?
- For the frequency calculated under (a) calculate currents  $I_1(t)$ ,  $I_2(t)$  and  $I_3(t)$ .
- Calculate active and reactive power supplied by the source.

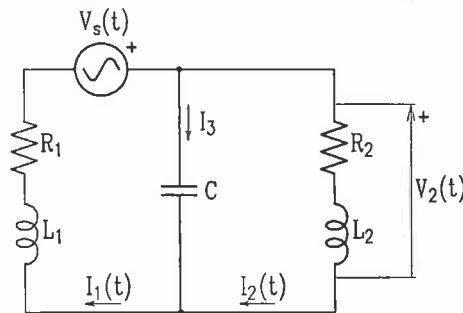


Figure 5: Circuit diagram for Question 5

**Question 6**

A diode bridge rectifier is used to provide a DC current to a  $50 \text{ k}\Omega$  resistive load. Rectifier will be supplied by an ideal AC voltage source ( $60 \text{ Hz}$ ,  $20 \text{ V}_{\text{RMS}}$ ).

- Draw the rectifier schematic diagram. Sketch the input voltage, the output voltage, the output current, and the current through each of the four rectifier diodes.
- Find the peak and the average current in the load.
- Sketch the input and the output voltage if the rectifier diode has on-state voltage drop of  $0.5 \text{ V}$ .
- Using a  $100 \Omega$  resistance, design an RC low-pass filter (for DC side) that can attenuate a  $120 \text{ Hz}$  sinusoidal voltage by  $20 \text{ dB}$  with respect to the DC gain.

**Question 7**

A logic platform controls a heating and air-conditioning system. It uses the following sensors for operation:

- A) Time elapsed from the last compressor turn-off instant (1 if the minimal time is exceeded)
- B) Over-temperature (1 if the ambient temperature is higher than  $t_{HI}$ )
- C) Under-temperature (1 if the ambient temperature is lower than  $t_{LO}$ )
- D) Heating function switch (1 if ON)
- E) Cooling function switch (1 if ON)
- F) Furnace over-temperature (1 if the furnace temperature is higher than  $t_{Furnace}$ )

The furnace should be turned on if the heating function switch is in the ON position and the ambient temperature is lower than the set value for heating  $t_{LO}$ . The compressor should be turned on if the cooling function switch is in the ON position and the ambient temperature is higher than the set value for cooling  $t_{HI}$ . Once the compressor is turned off there is a minimum time delay before it is allowed to turn on again. The fan should be ON if the compressor is ON or if the furnace temperature is higher than  $t_{Furnace}$ .

- a) Design the logic circuit that controls the furnace.
- b) Design the logic circuit that controls the compressor.
- c) Construct the truth table for controlling the fan.
- d) Design the logic circuit that controls the fan.

**Note:**

Any gate type can be used to construct the logic circuits.