

National Exams May 2012  
04-BS-4 Electric Circuits and Power

**3 hours duration**

**Notes:**

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of assumptions made;
2. Candidates may use one of two calculators, a Casio or Sharp approved models. This is a **Closed Book** exam. **One** aid sheet written on both sides is permitted.
3. Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.
4. All questions are of equal value.

**Question 1**

In the DC circuit of Figure 1 assume the following:  $R_1 = 20\ \Omega$ ,  $R_2 = 2\ \Omega$ ,  $R_3 = 4\ \Omega$ ,  $R_4 = 20\ \Omega$ ,  $V_5 = 99\ \text{V}$ , and  $V_6 = 100\ \text{V}$ .

- Write Kirchhoff's current law equations for nodes A, B, and C. Write Kirchhoff's voltage law equations for loops ACBA, ACDA, and ABCDA;
- Using Kirchhoff's laws calculate currents  $I_1$  and  $I_4$ ;
- Calculate voltage  $V_{CD}$ ;
- Calculate power dissipated in resistor  $R_4$ ?

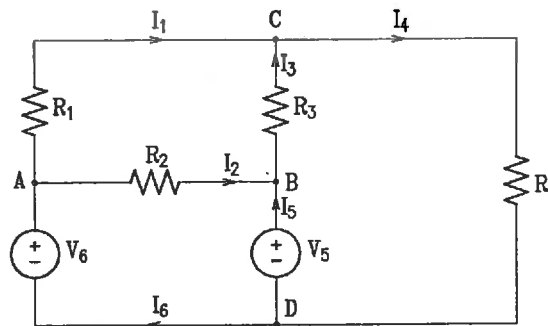


Figure 1: Circuit diagram for Question 1

**Question 2**

Consider the circuit of Figure 2. Known parameters are:  $R_1 = 2.5\ \text{k}\Omega$ ,  $R_2 = 2\ \text{k}\Omega$ ,  $R_3 = 50\ \Omega$ ,  $R_4 = 350\ \Omega$ ,  $C_4 = 7\ \mu\text{F}$ ,  $R_5 = 40\ \text{k}\Omega$ ,  $R_6 = 10\ \text{k}\Omega$ ,  $I_s = 1\ \text{mA}$ ,  $V_{s1} = 10\ \text{V}$ , and  $V_{s2} = 40\ \text{V}$ . Determine the following:

- Thevenin equivalent resistance with respect to the load terminals;
- Thevenin equivalent voltage with respect to the load terminals;
- Determine the load resistance for the maximum power transfer. Determine the maximum power transferred to the load.
- Determine the power transferred to the load if the load resistance is  $R_L = 72\ \Omega$ .

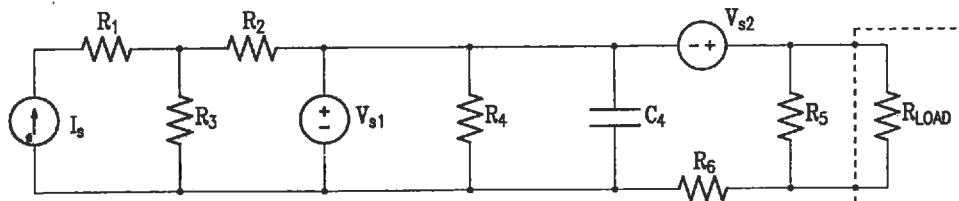


Figure 2: Circuit diagram for Question 2

**Question 3**

In the circuit of Figure 3, parameters are:  $R = 10\ \Omega$ ,  $L_1 = 10\ \text{mH}$ ,  $L_2 = 5\ \text{H}$ ,  $C_1 = 10\ \mu\text{F}$ ,  $C_2 = 2\ \mu\text{F}$ , and  $V_s(t) = 100 \cos(\omega t)\ \text{V}$ .

- Assume that the source frequency is 60 Hz. Calculate current  $i(t)$  and voltage  $v_1(t)$ .
- For the source frequency 60 Hz, Calculate active and reactive power supplied by the source.
- Determine the source frequency so that current  $i(t)$  is in phase with the voltage  $v_2(t)$ . What is this frequency called?
- Determine the source frequency so that the power supplied by the source is zero.

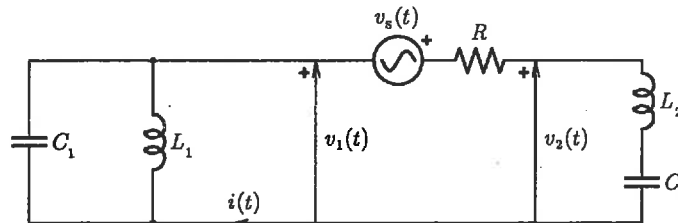


Figure 3: Circuit diagram for Question 3

**Question 4**

In the circuit of Figure 4  $R_1 = 3\ \Omega$ ,  $R_2 = 3\ \Omega$ ,  $R_3 = 6\ \Omega$ ,  $R_4 = 4\ \Omega$ ,  $R_5 = 4\ \Omega$ ,  $R_6 = 8\ \Omega$ ,  $L = 20\ \text{mH}$ , and  $V_s = 12\ \text{V}$ . The switch S is closed for a long time. At  $t = 0\ \text{s}$ , the switch S opens.

- Calculate the voltage across the resistor  $R_4$  and the inductor current in steady-state while the switch S is closed.
- What is the energy stored in the inductor at  $t = 0_-\ \text{s}$ .
- Calculate the time constant of the circuit when the switch is open;
- Plot current  $I_L(t)$  from  $t = -5\ \text{ms}$  to  $t = 25\ \text{ms}$ ;

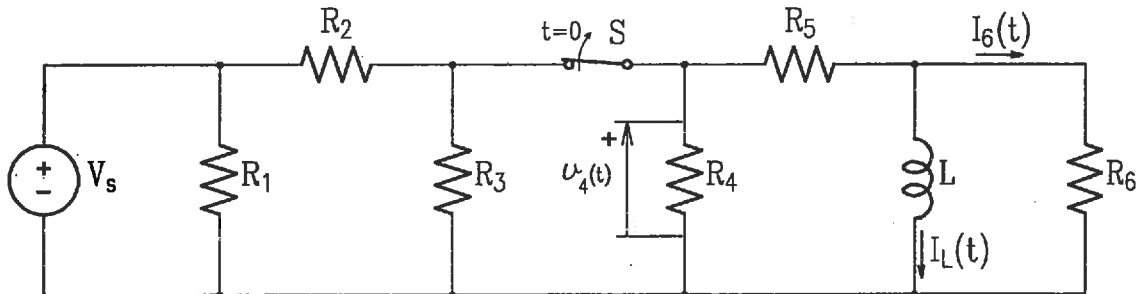


Figure 4: Circuit diagram for Question 4

**Question 5**

A magnetic core is shown in Figure 5. Consider that the cross section is uniform and equal to  $100 \text{ mm}^2$ , relative permeability  $\mu_r = 2000$ , number of winding turns  $N = 100$  and current  $I = 1 \text{ A}$  ( $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ ).

- Compute the magnetomotive force.
- Calculate the equivalent reluctance of each segment of the magnetic circuit.
- Draw the analog circuit representation of the magnetic circuit from Figure 5.
- Calculate the magnetic flux, flux density and magnetic field intensity in the air gap.

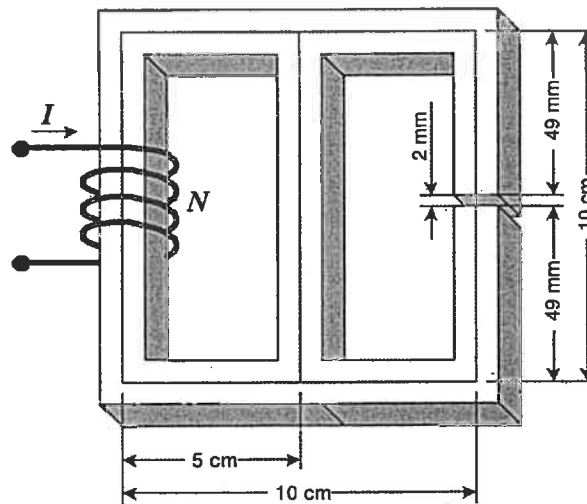


Figure 5: Magnetic core for Question 5

**Question 6**

A half-wave diode rectifier is used to provide a DC current to a  $50 \text{ k}\Omega$  resistive load. Rectifier is supplied by an ideal AC voltage source ( $50 \text{ Hz}$ ,  $20 \text{ V}_{\text{RMS}}$ ).

- Draw the rectifier schematic diagram. Sketch the input voltage, the output voltage, the output current, and the current through each of the rectifier diodes.
- Find the peak and the average current in the load.
- Sketch the input and the output voltage, if the rectifier diode has on-state voltage drop of  $0.4 \text{ V}$ .
- Using a  $50 \Omega$  resistance, design an RC low-pass filter (for DC side) that can attenuate a  $100 \text{ Hz}$  sinusoidal voltage by  $20 \text{ dB}$  with respect to the DC gain.

**Question 7**

A logic platform provides the wind turbine blade pitch (angle) control. To operate, it uses the following sensors:

- A) *Emergency stop* switch (1 if pressed)
- B) Limit switch for *Full-speed* position (1 if reached)
- C) Limit switch for *Vane* position (1 if reached)
- D) Turbine *Ready* signal(1 if ready)
- E) Wind speed upper limit (1 if wind speed is too high)
- F) Wind speed lower limit (1 if wind speed is too low)
- G) Rotor speed limit (1 if rotor speed is too high)

The wind turbine rotor blades should be in *Vane* position when the turbine is not operational and should be in *Full-speed* position under normal operating conditions. Rotor blade pitch is achieved by means of special servo motors that respond to commands:

- a) Up (initiate blade movement toward *Full-speed* position)
- b) Down (initiate normal blade movement toward *Vane* position)
- c) Fast Down (initiate fast blade movement toward *Vane* position)

The *Emergency Stop Condition* is when the wind speed is too high, turbine is not *Ready*, or *Emergency stop* button is pressed. When emergency stop condition is detected blades should move fast to *Vane* position.

Rotor speed should never exceed the maximum rotor speed. If the maximum rotor speed limit is reached, the blade should move toward *Vane* position. The blade movement should stop when the rotor speed drops below the speed limit.

If the wind speed is too low, and turbine is ready, blades should move to *Vane* position.

Neglect the changing wind conditions.

- a) Design a logic circuit that initiates normal start and brings blades to *Full-speed* position.
- b) Design a logic circuit that handles the *Emergency Stop Condition*.
- c) Design a logic circuit that assures that the turbine speed does not exceed the speed limit.
- d) Design a logic circuit that initiates normal stop due to too low wind speed.

**Note:**

All kinds of gates could be used to construct the logic circuits.