

**National Exam December, 2013**

**07-Elec-A1 Circuits**

**3 hours duration**

**NOTES:**

1. **No questions to be asked.** If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any logical assumptions made.
2. Candidates may use one of two calculators, a Casio FX or Sharp EL . **No programmable models** are allowed.
3. This is a **closed book** examination.
4. Any **five questions** constitute a complete paper. Please indicate in the front page of your answer book which questions you want to be marked. **If not indicated, only the first five questions as they appear in your answer book will be marked.**
5. All questions are of equal value.
6. **Laplace Table** is given in the last page of this question paper.

**Q1: (a)** Write the node voltage equations at nodes 1 and 2 of the dc circuit shown in Figure-1.

Solve node voltages  $V_1$  and  $V_2$ . [12]

**(b)** After solving the node voltages, calculate the power dissipations in  $5\Omega$  and  $4\Omega$  resistances. [8]

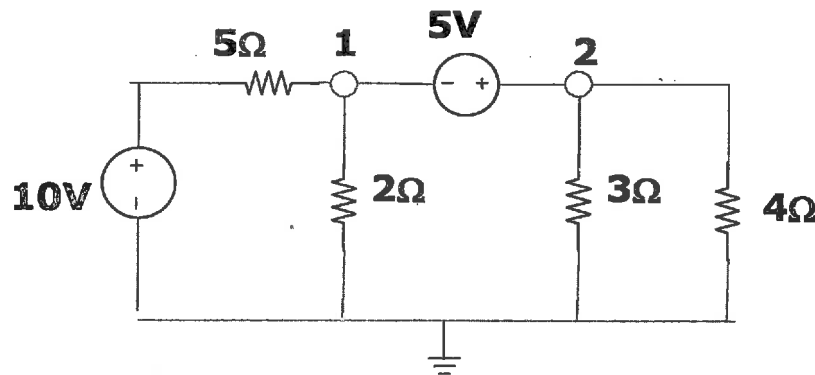


Figure-1

**Q2:** In the circuit shown in Figure-2, the switch was in position-a for a long time. At time  $t=0$ , the switch is moved to position-b.

(i) At  $t=0^+$ , calculate  $V_c(+)$ . [5]

(ii) Solve  $V_c(t)$  at  $t \geq 0$ . [10]

(iii) Find  $V_c$  at  $t = 2$  sec. [5]

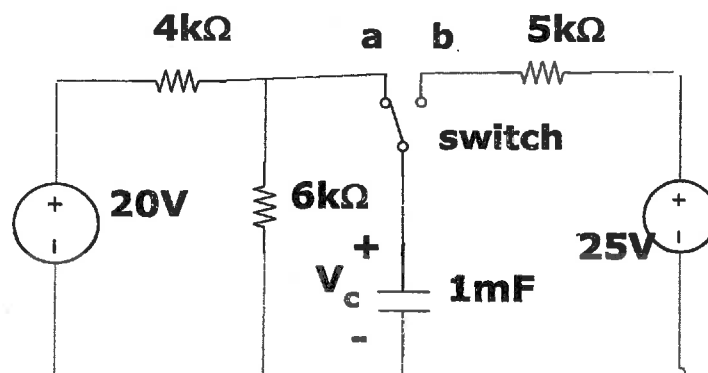


Figure-2

- Q3: (a) Write the current mesh equations of the circuit shown in Figure-3. [10]  
 (b) Solve the mesh currents. [5]  
 (c) After solving the mesh currents, calculate the voltage,  $V_o$  across the resistance  $4\Omega$ . [5]

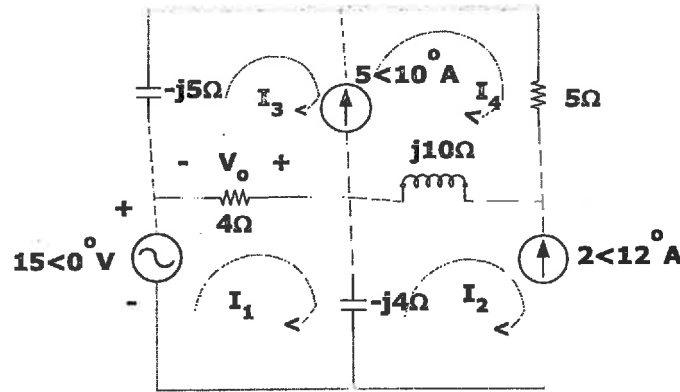


Figure-3

- Q4: (a) Calculate the Thevenin's equivalent circuit ( $V_{th}$  and  $Z_{th}$ ) at terminals A-B of the of the circuit shown in Figure-4. [12]  
 (b) What should be the value of load impedance,  $Z_{load}$  at A-B to get maximum Power output in  $Z_{load}$ . [2]  
 (c) What is the maximum power dissipation in the load  $Z_{load}$ ? [6]

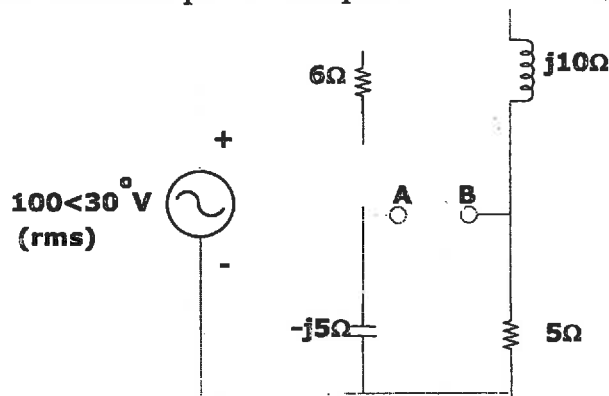


Figure-4

- Q5: (a) Calculate the resonance frequency,  $f_0$  of the circuit shown in Figure-5. [12]  
 (b) Calculate the cut-off frequencies  $f_1$  and  $f_2$  of the circuit. [8]

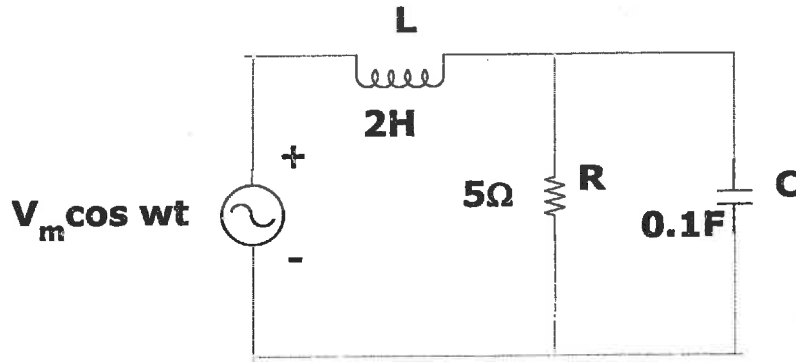


Figure-5

Q6: The circuit shown in Figure-6 has initial capacitor voltage of 8V, and initial Inductor current of 4A.

- (a) Draw Laplace transformed circuit of the network. [10]  
 (b) Calculate Laplace inductor current,  $I_L(s)$ . [5]  
 (c) Solve  $i_L(t)$ . [5]

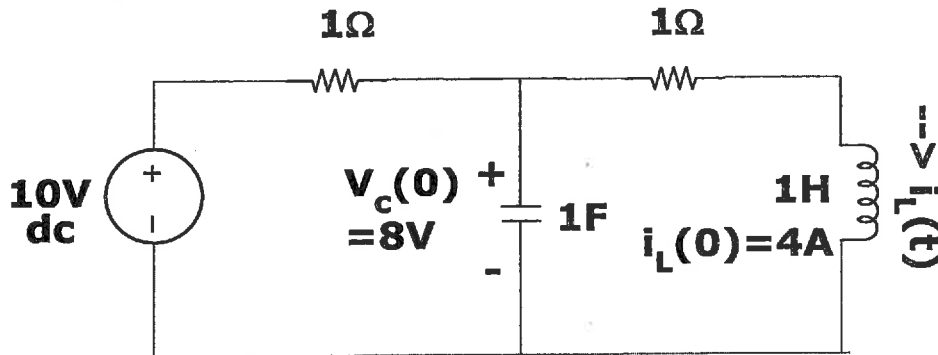


Figure-6

### Appendix

Some useful Laplace Transforms:

<u>f(t)</u>	→	<u>F(s)</u>
$Ku(t)$		$K/s$
$t^n$		$\frac{n!}{s^{n+1}}$
$e^{-at} u(t)$		$1/(s+a)$
$\sin \omega t \cdot u(t)$		$\omega / (s^2 + \omega^2)$
$\cos \omega t \cdot u(t)$		$s / (s^2 + \omega^2)$
$e^{-at} \sin \omega t$		$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$		$\frac{(s+a)}{(s+a)^2 + \omega^2}$
$\frac{df(t)}{dt}$		$sF(s) - f(0^-)$
$\frac{d^2 f(t)}{dt^2}$		$s^2 F(s) - s f(0^-) - f'(0^-)$
$\int_{-\infty}^t f(q) dq$		$\frac{F(s)}{s} + \int_{-\infty}^0 f(q) dq$