

National Exams December 2015  
04-BS-4 Electric Circuits and Power

3 hours duration

Notes:

1. If doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of assumptions made;
2. Candidates December use one of two calculators, a Casio or Sharp approved models. This is a **Closed Book** exam. **One** aid sheet written on both sides is permitted.
3. Any five questions constitute a complete paper. Only the first five questions as they appear in your answer book will be marked.

Marking Scheme

- Question 1: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 2: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 3: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 4: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 5: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 6: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.  
Question 7: (a) 5 marks, (b) 5 marks, (c) 5 marks, (d) 5 marks.

**Question 1**

In the DC circuit of Figure 1 assume the following:  $R_1 = 1\ \Omega$ ,  $R_2 = 2\ \Omega$ ,  $R_3 = 1\ \Omega$ ,  $R_4 = 5\ \Omega$ ,  $R_5 = 5\ \Omega$ ,  $R_6 = 15\ \Omega$ ,  $V_{s1} = 30\ \text{V}$ ,  $V_{s5} = 25\ \text{V}$ , and  $I_s = 5\ \text{A}$ .

- Write Kirchhoff's Current Law (KCL) equations for nodes A, B, and C.
- Write Kirchhoff's Voltage Law (KVL) equations for loops ABDA and ABCA.
- Calculate the voltage across resistor  $R_2$ .
- Calculate current  $I_2$  and the power dissipated in resistor  $R_2$ .

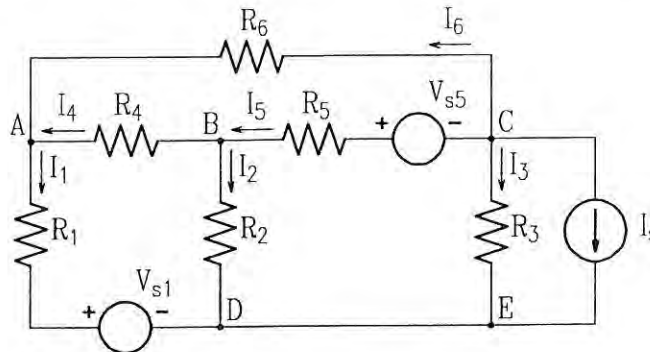


Figure 1: Circuit diagram for Question 1

**Question 2**

Consider the circuit of Figure 2. Known parameters are:  $R_1 = 12.5\ \text{M}\Omega$ ,  $R_2 = 22.5\ \text{k}\Omega$ ,  $R_3 = 300\ \text{k}\Omega$ ,  $R_4 = 100\ \text{k}\Omega$ ,  $R_5 = 10\ \text{k}\Omega$ ,  $R_6 = 10\ \text{k}\Omega$ ,  $R_7 = 5\ \text{k}\Omega$ , and  $V_s = 20\ \text{V}$ . Determine the following:

- Thevenin equivalent resistance seen by the load;
- Thevenin equivalent voltage seen by the load;
- Power transferred to the load if the load resistance is  $R_L = 100\ \Omega$ .
- Determine the load resistance for the maximum power transfer. Determine the power transferred to the load in this case.

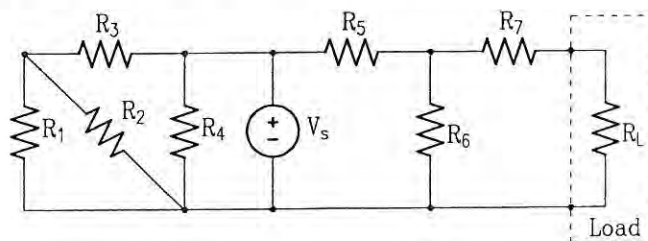


Figure 2: Circuit diagram for Question 2

**Question 3**

In the circuit of Figure 3  $R_1 = 3\ \Omega$ ,  $R_2 = 3\ \Omega$ ,  $R_3 = 6\ \Omega$ ,  $R_4 = 4\ \Omega$ ,  $R_5 = 4\ \Omega$ ,  $R_6 = 8\ \Omega$ ,  $L = 20\ \text{mH}$ , and  $V_s = 12\ \text{V}$ . The switch  $S$  is closed for a long time. At  $t = 0\ \text{s}$ , the switch  $S$  opens.

- Calculate the voltage across the resistor  $R_4$  and the inductor current in steady-state while the switch  $S$  is closed.
- What is the energy stored in the inductor at  $t = 0_-$  s.
- Calculate the time constant of the circuit when the switch is open;
- Plot the current  $I_L(t)$  from  $t = -5\ \text{ms}$  to  $t = 25\ \text{ms}$ ;

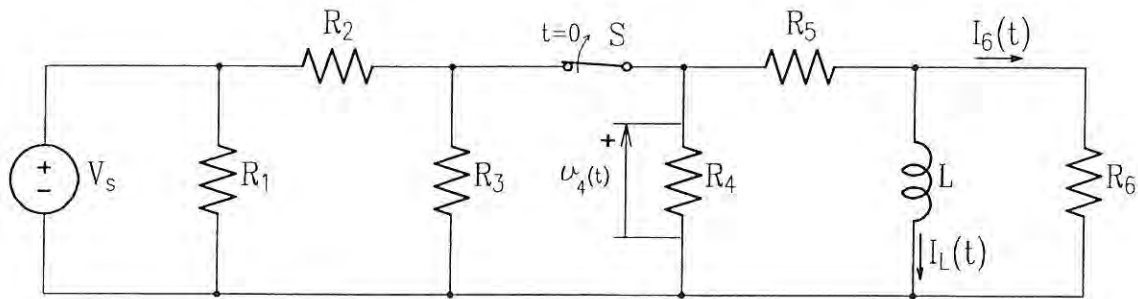


Figure 3: Circuit diagram for Question 3

**Question 4**

In the circuit of Figure 4 assume the following:  $L_1 = 160\ \text{mH}$ ,  $L_2 = 80\ \text{mH}$ ,  $R_1 = 5\ \Omega$ ,  $R_2 = 2\ \Omega$ ,  $C = 20\ \text{mF}$ , and  $v_s(t) = \sqrt{2} 10 \cos(100t)\ \text{V}$ . Assume that the circuit is in a steady-state operating condition. Calculate the following:

- Impedances  $Z_{L1}$ ,  $Z_{L2}$ , and  $Z_C$ ;
- Voltage phasor  $\underline{V}_1$ ;
- Current phasor  $\underline{I}_1$ ;
- Capacitor current in time-domain.

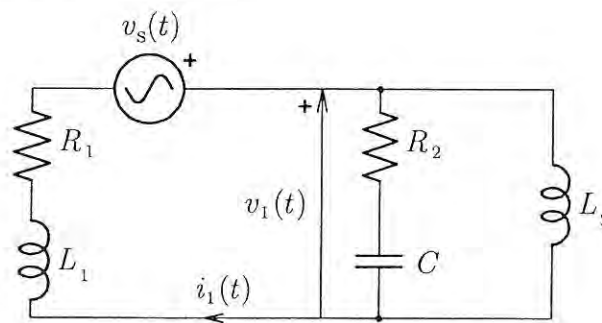


Figure 4: Circuit diagram for Question 4

**Question 5**

A magnetic core is shown in Figure 5. Assume that the core cross section is uniform and equal to  $100 \text{ mm}^2$ , relative permeability  $\mu_r = 2000$ , number of winding turns  $N = 100$  and current  $I = 1 \text{ A}$  ( $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ ).

- Calculate the magnetomotive force.
- Calculate the equivalent reluctance of each part of the magnetic circuit.
- Draw the analog circuit representation of the magnetic circuit from Figure 5.
- Calculate the magnetic flux, flux density and magnetic field intensity in the air gap.

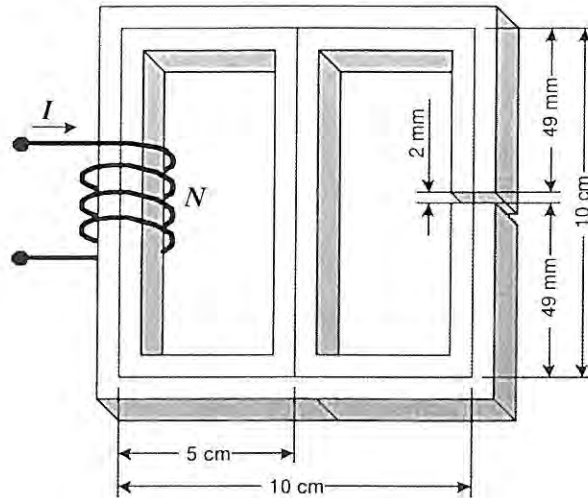


Figure 5: Magnetic core for Question 5

**Question 6**

A full-wave diode rectifier is used to provide a DC current to a  $50 \text{ k}\Omega$  resistive load. Rectifier is supplied by an ideal AC voltage source ( $60 \text{ Hz}$ ,  $110 \text{ V}_{\text{RMS}}$ ) and a transformer with the center-tapped secondary (transformer turns-ratio is  $110/10/10 \text{ V}$ ).

- Draw the rectifier schematic diagram. Sketch the input voltage, the output voltage, the output current, and the current through each of the rectifier diodes.
- Find the peak and the average current in the load.
- Sketch the input and the output voltage waveforms, if the rectifier diode has on-state voltage drop of  $0.5 \text{ V}$ .
- Using a  $100 \Omega$  resistance, design an RC low-pass filter (for DC side) that can attenuate a  $60 \text{ Hz}$  sinusoidal voltage by  $20 \text{ dB}$  with respect to the DC gain.

**Question 7**

A logic platform controls a two-stage heating and air-conditioning system. It uses the following sensors for operation:

- A) Time elapsed from the last compressor turn-off instant (1 if the minimal rest time  $t_{\text{REST}}$  is exceeded)
- B) Time elapsed from the moment the fan started blowing (1 if the Stage 1 time  $t_{\text{Stage1}}$  is exceeded)
- C) Over-temperature (1 if the ambient temperature is higher than  $t_{\text{HI}}$ )
- D) Under-temperature (1 if the ambient temperature is lower than  $t_{\text{LO}}$ )
- E) Heating function switch (1 if ON)
- F) Cooling function switch (1 if ON)
- G) Furnace over-temperature (1 if the furnace temperature is higher than  $t_{\text{Furnace}}$ )

The furnace should be turned on if the heating function switch is in the ON position and the ambient temperature is lower than the set value for heating  $t_{\text{LO}}$ . The compressor should be turned on if the cooling function switch is in the ON position and the ambient temperature is higher than the set value for cooling  $t_{\text{HI}}$ . Once the compressor is turned off there is a minimum time delay before it is allowed to turn on again. The fan should be ON if the compressor is ON or if the furnace temperature is higher than  $t_{\text{Furnace}}$ . Fan always turns ON at low-speed and continues with low-speed operation until the set time  $t_{\text{Stage1}}$  is exceeded or desired temperature is reached. If the desired temperature is not reached and the time allocated to Stage 1 expired, the fan switches to high-speed operation.

- a) Design the logic circuit that controls the furnace.
- b) Design the logic circuit that controls the compressor.
- c) Design the logic circuit that sets the fan in low-speed mode.
- d) Design the logic circuit that sets the fan in high-speed mode.

**Note:**

Any gate type can be used to construct the logic circuits.