

National Exams May 2015

04-BS-8, Digital Logic Circuits

3 hours duration

NOTES:

1. If a doubt exists as to the interpretation of any question, the candidate is urged to submit with the answer paper, a clear statement of any assumption made with the answer of the question.
2. Candidates may use one of two calculators, the Casio or Sharp approved models. This is a closed book examination; however, candidates are allowed to bring one hand-written information sheet (8.5" X 11") of self-prepared notes.
3. This paper contains **FIVE (5)** questions and comprises **SIX (6)** pages.
4. Any **FOUR (4)** questions constitute a complete paper. Only the first four questions as they appear in your answer book will be marked.
5. All questions are of equal marks. Total marks = 100
6. Each question carries 25 marks and the marks for each part of questions are indicated in brackets.
7. A PAL16L8 Data sheet is provided in the Appendix. It can be used to provide the solution of Question 2, part (b) and should be attached to your answer sheet.

1. A digital system is to be developed that can detect a sequence of bits at its single-bit input serial channel. The sequence detector receives data stream bits (**DS**) in a serial way. A synchronizing clock that shifts the data-bits is also available along with the data stream bits. Each **DS** bit spans between consecutive positive transitions of the clock. Design the sequence detector as a sequential circuit such that its output, **out** goes to logic **HIGH** during the 5th bit of a valid sequence, **11010**. The sequence always starts with the most significant bit.
 - (a) Draw the state diagram and state table for the sequence detector sequential circuit.

(12 marks)
 - (b) Design the sequence detector by using suitable edge-triggered (negative or positive) JK flip-flops.

(13 marks)

2. (a) Identify the main differences between ROM and FPGA devices that are used to implement digital logic circuits.

(6 marks)

- (b) Implement the following four Boolean expressions by using a PAL16L8 programmable logic device.

$$\mathbf{F1}(w, x, y, z) = \sum \mathbf{m}(0, 2, 4, 6, 7, 9, 11, 13)$$

$$\mathbf{F2}(w, x, y, z) = \sum \mathbf{m}(0, 1, 4, 6, 8, 10, 14)$$

$$\mathbf{F3}(w, x, y, z) = \sum \mathbf{m}(1, 3, 4, 7, 9, 12, 15)$$

$$\mathbf{F4}(w, x, y, z) = \sum \mathbf{m}(1, 5, 6, 8, 14, 15)$$

Attach the duly completed PAL16L8 diagram to your answer book.

(12 marks)

- (c) Implement the Boolean function, **F4**(w, x, y, z) in part (b) by using a 3-to-8 decoder as given in the Appendix and the minimum number of gates.

(7 marks)

3. Provide a brief answer for the following questions with justification.

(a) For 2's complement representation of 8-bit size, which of the following values is equal to the decimal value (-49). Justify your answer.

- i). $(10110001)_2$ ii). $(11001111)_2$
iii). $(00110001)_2$

(6 marks)

(b) Which of the following binary values is closest to the decimal value $(1.6)_{10}$. Justify your answer.

- i). $(1.1)_2$ ii). $(1.011)_2$
iii). $(1.110001)_2$ iv). $(1.101)_2$

(6 marks)

(c) If $A = 1$, $B = 0$, and $C = 0$, then find X , where $X = (\overline{A \oplus B}) + C$

(3 marks)

(d) Identify the clocked flip-flop described in the following characterization table.

Inputs		Output
A	B	Q_{n+1}
0	0	Q_n
1	0	0
0	1	$\frac{1}{Q_n}$
1	1	Q_n

(6 marks)

(e) Considering a 2-Kbyte size memory that facilitates a byte-wide read and write, which of the following information is correct.

- i). 2000 address lines and 8 data lines.
ii). 12 address lines and 8 data lines.
iii). 13 address lines and 8 data lines.
iv). 11 address lines and 8 data lines.

Justify your answer

(4 marks)

4. (a) Show how a D-type flip-flop can be constructed by using an SR flip-flop and other logic gates. Draw the complete logic diagram of the circuit. (6 marks)
- (b) Design and implement a 4-bit counter that counts down in sequence (---- 14, 12, 10, 8, 6, 4, 2, 0, 14 ----) by using the minimum number of D-type flip-flops and basic logic gates. Show your complete design with full details including state diagram, state table, simplification of next state equations and a counter with the minimal hardware. (19 marks)

5. A combinational logic circuit is needed to multiply a 3-bit binary number ($A_2A_1A_0$) by a constant 3_{10} , as shown in Figure Q5.


 


Figure Q5


- (a) Determine the number of input and output signals for multiplicand, multiplier and result (m , n and r). (3 marks)
- (b) Construct the truth table of the circuit indicating the input and output variables. (7 marks)
- (c) Simplify the output function using Boolean algebra and write the reduced Boolean functions of the output. (6 marks)
- (d) Simplify the output function using K-map and write the reduced output function. Then implement the Boolean function by using the minimum number of NAND gates. (9 marks)

APPENDIX
PAL16L8

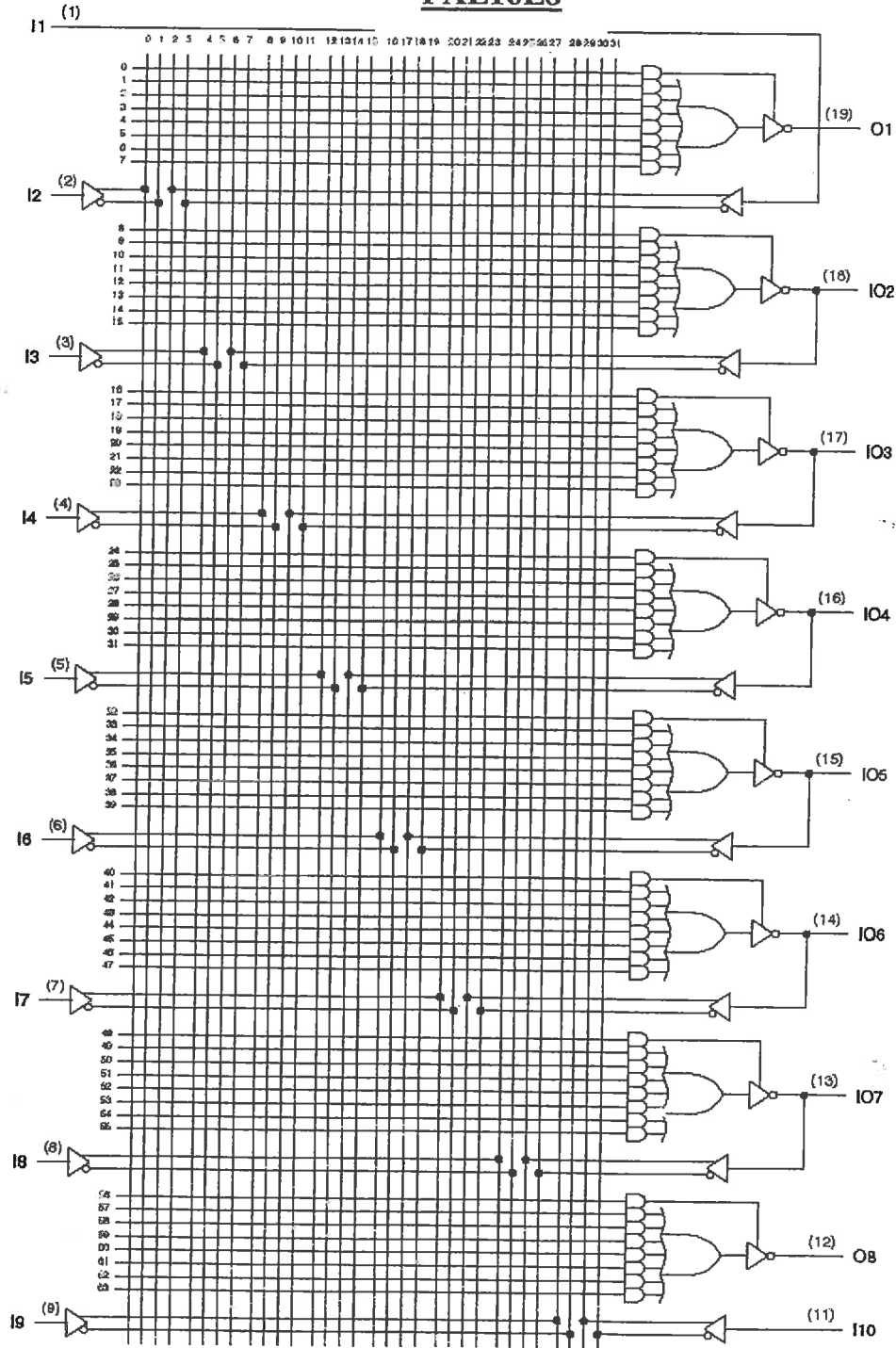

Decoder Data Sheet

74LS138: 3-to-8 Decoder

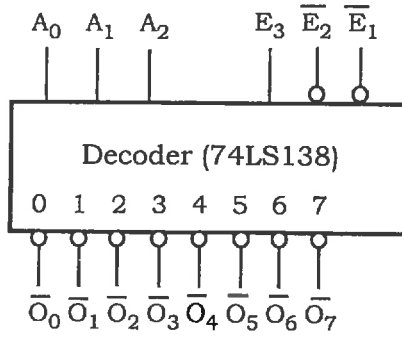

Inputs			
$\overline{E_1}$	$\overline{E_2}$	E_3	
0	0	1	Respond to input code $A_2A_1A_0$
1	x	x	Disabled - all HIGH
x	1	x	Disabled - all HIGH
x	X	0	Disabled - all HIGH