

National Exams May 2015

98-Comp-A1, Electronics

3 hours duration

NOTES:

1. If doubt exists as to the interpretation of any question, the candidate is urged to indicate, with the answer, a clear statement of any assumptions made.
2. This is a OPEN BOOK exam.
Any non-communicating calculator is permitted.
3. FIVE (5) questions constitute a complete exam paper.
The first 5 questions as they appear in the answer book will be marked.
4. Each question is of equal value.

Question 1 (20 marks)

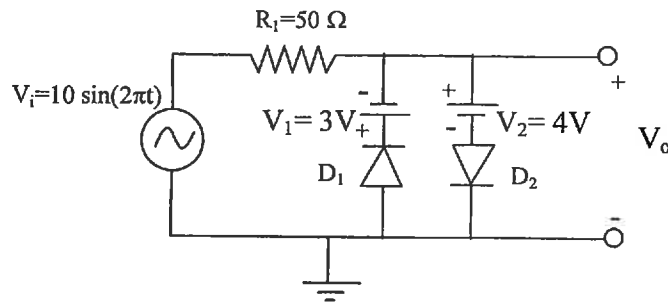


Figure 1. The diodes have a voltage drop $V_D=0.7V$ in forward bias.

For the circuit shown in Figure 1:

- Sketch V_i and V_o as a function of time, indicating peak voltages.
- How should D_1 be rated for power consumption?
- What is the peak current in R_1 ?

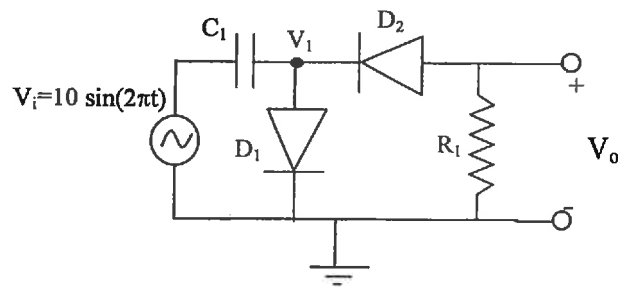


Figure 2. The diodes have a voltage drop $V_D=0.7V$ in forward bias.

For the circuit shown in Figure 2:

- Sketch the output waveform $V_o(t)$ in steady state. Label key voltages and times, and indicate changes in operating region for the diodes.

Question 2 (20 marks)

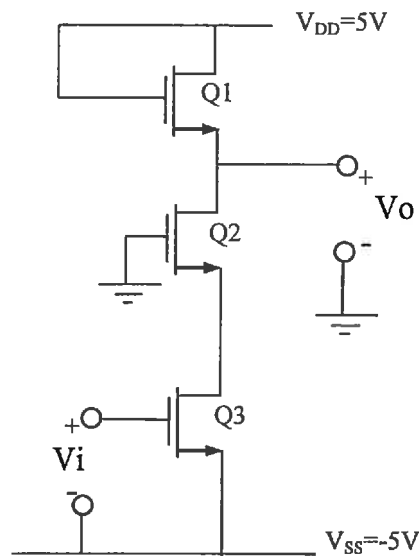


Figure 3. $k_n' = \mu_n C_{ox} = 1 \text{ mA/V}^2$, $W/L = 10$, $V_{tn} = 1 \text{ V}$, $|V_A| = 100 \text{ V}$

For the circuit shown in Figure 3:

- a) For $V_i = 2 \text{ V}$ what is the current through Q3?
- b) What is V_{DS} for Q1?
- c) Draw a small signal equivalent model for the circuit.
- d) What is the small signal AC gain of the circuit?

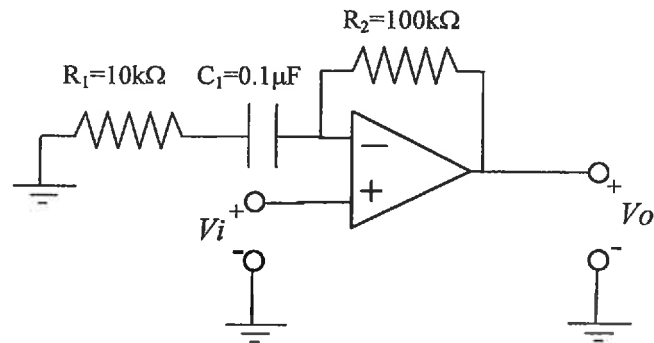
Question 3 (20 marks)

Figure 4.

For the circuit shown in Figure 4:

- Derive the transfer function $\frac{V_o(j\omega)}{V_i(j\omega)}$ for the circuit shown in Figure 4, assuming the op-amp is ideal.
- Sketch the frequency response, indicating the 3dB frequency for this circuit.
- If $V_i(t) = 10\sin(120\pi t)$ V, find $V_o(j\omega)$.
- If $V_i(t) = 10\sin(120\pi t)$ V, find $V_o(t)$.

Question 4(20 marks)

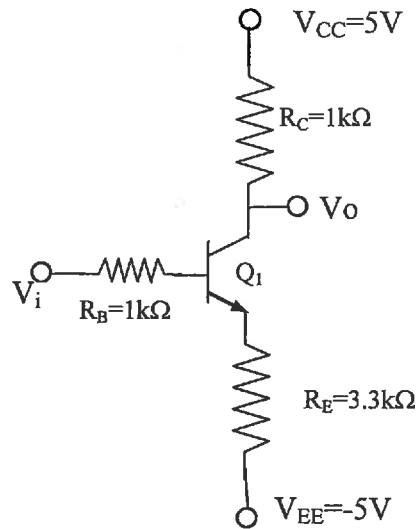


Figure 5. $V_{be}=0.7V$ (active), $V_{ce}=0.2V$ (saturation), $\beta=100$.

For the circuit shown in Figure 5:

- If $V_i=0V$ DC, find the DC bias point for Q1?
- Draw the small signal equivalent circuit and evaluate the small signal AC voltage gain.
- Sketch I_c vs V_{ce} and show the operating point for the transistor.
- How would you change the bias to obtain maximum signal swing?

Question 5 (20 marks)

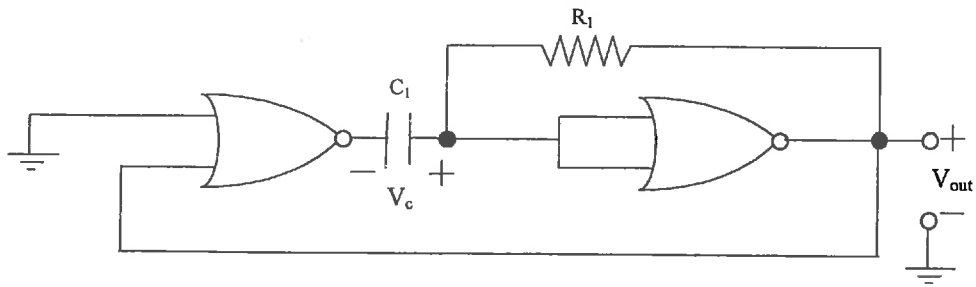


Figure 6. Assume the gates are ideal and switch at $V_{DD}/2$.

For the circuit shown in Figure 6:

- Explain the operation of this circuit.
- Sketch the waveforms $V_c(t)$ and $V_{out}(t)$.
- Find an expression for $V_c(t)$.
- Find the period of the waveform if $R_1=10\text{ k}\Omega$ and $C_1=10\text{ nF}$.

Question 6 (20 marks)

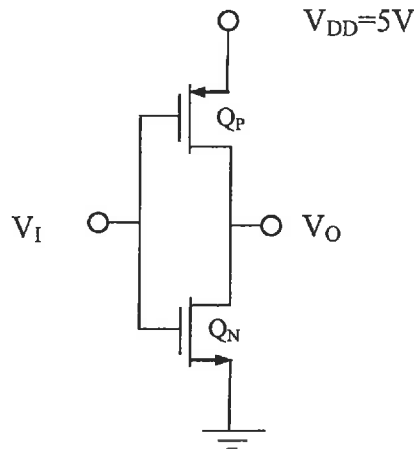


Figure 7. $k_n' = 50 \mu\text{A}/\text{V}^2$, $k_p' = 20 \mu\text{A}/\text{V}^2$, $V_{tn} = -V_{tp} = 1\text{V}$, $C_{ox} = 1\text{fF}/\mu\text{m}^2$, $V_{DD} = 5\text{V}$.

- a) If the minimum gate length for this technology is $1 \mu\text{m}$, size Q_N and Q_P to obtain a symmetric transfer characteristic.
- b) Estimate the maximum capacitance this circuit can drive with a propagation delay of less than 200 ps.

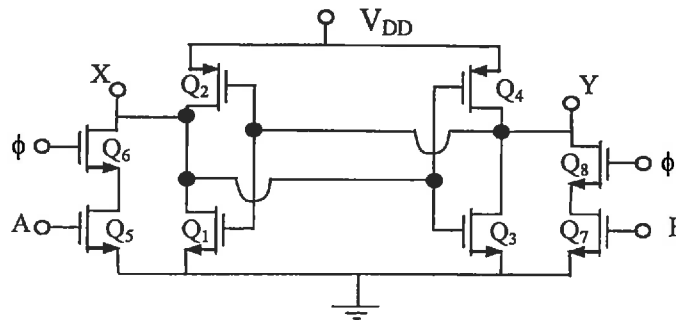


Figure 8.

For the circuit shown in Figure 8:

- c) Determine outputs X and Y for all possible inputs A and B. ϕ is a clock signal.
- d) If Q_1 and Q_2 are sized as in part a), find a minimum size for Q_5 and Q_6 that will ensure X can be pulled down to $V_{DD}/2$ or lower.

Question 7 (20 marks)

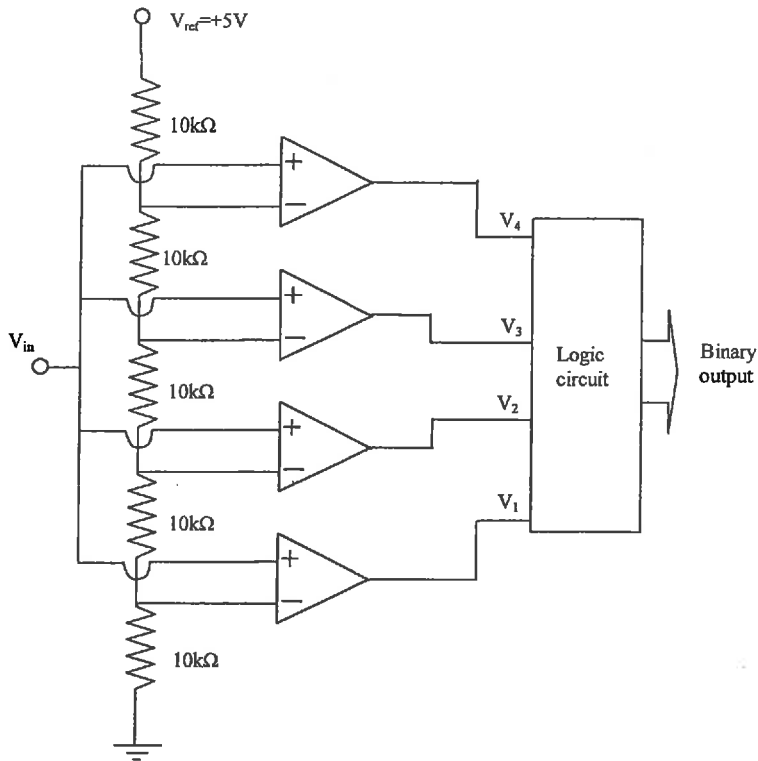


Figure 9.

- What is a common name for the ADC circuit shown in Figure 9? What is a principal advantage of this circuit over other ADC implementations?
- What are the analog voltages at each of the comparator negative inputs? If $V_{in}=3V$ what are the logic values for V_1 through V_4 ?
- List all possible combinations of V_1 - V_4 and the corresponding binary output.
- In an integrated circuit, how could V_{ref} be generated?

Marking Scheme

1. 20 marks total (4 parts, 5 marks each)
2. 20 marks total (4 parts, 5 marks each)
3. 20 marks total (4 parts, 5 marks each)
4. 20 marks total (4 parts, 5 marks each)
5. 20 marks total (4 parts, 5 marks each)
6. 20 marks total (4 parts, 5 marks each)
7. 20 marks total (4 parts, 5 marks each)